

# Electronics 1: Chapter 2 figs

Alan Robert Clark

April 19, 2022

Note that the source code for the figs can be seen by clicking the pic. You will need to use your Browser's BACK button to return to this page.

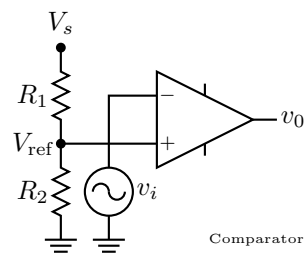


Figure 1: The Comparator

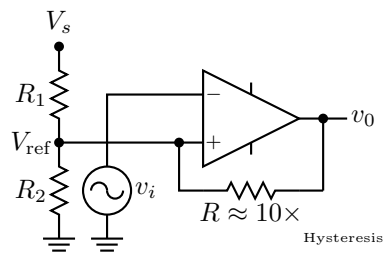


Figure 2: Positive Feedback causes state-dependant thresholds

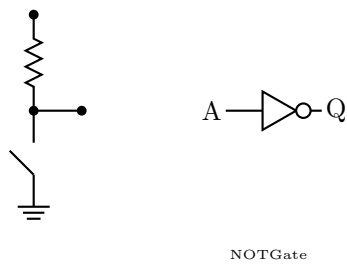


Figure 3: An Inverter

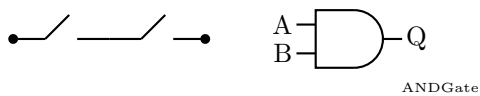


Figure 4: The AND Gate

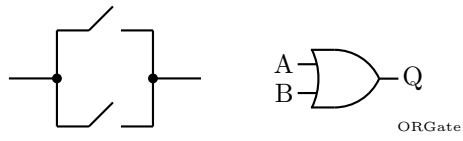


Figure 5: The OR Gate

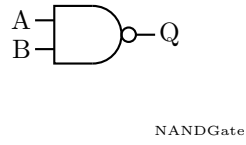


Figure 6: The NAND Gate

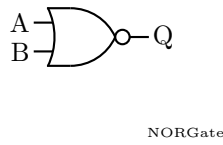


Figure 7: The NOR Gate.

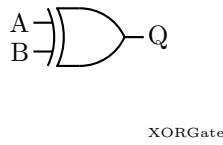


Figure 8: The XOR Gate

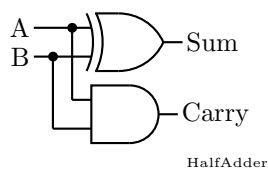


Figure 9: A Half Adder

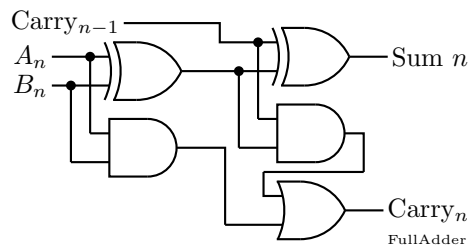


Figure 10: A Full Adder

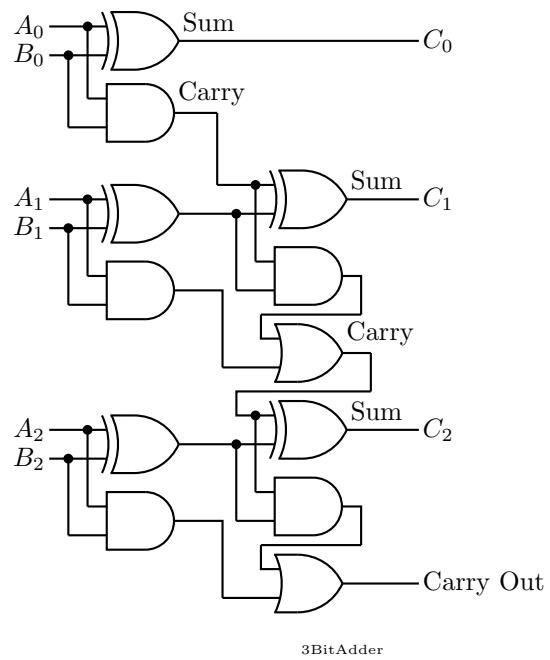


Figure 11: 3 Bit Adder!

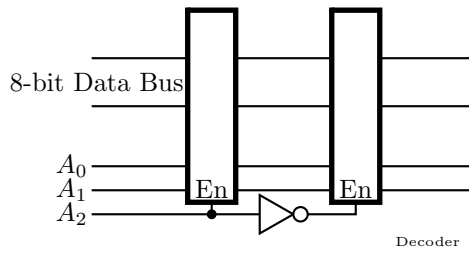


Figure 12: Simplest decoder to select between two 4-byte memories

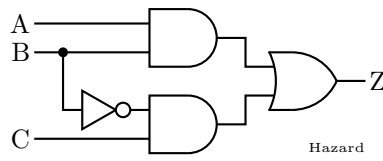


Figure 13: Timing Hazard.

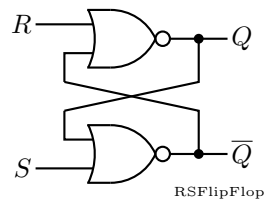


Figure 14: The RS (Reset-Set) Flip Flop

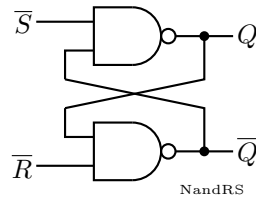


Figure 15: A Nand-based RS Flip Flop.

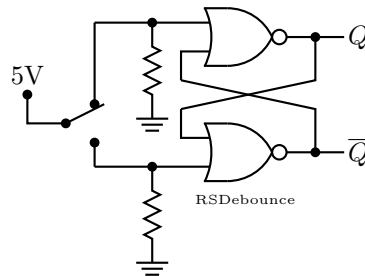


Figure 16: An RS Flip Flop used in debouncing

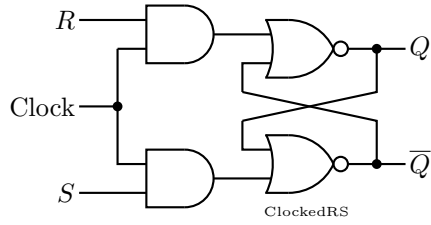


Figure 17: A Clocked RS Flip Flop

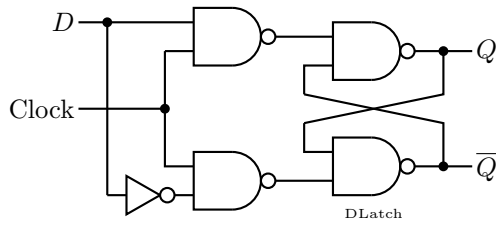


Figure 18: NAND gate D Latch

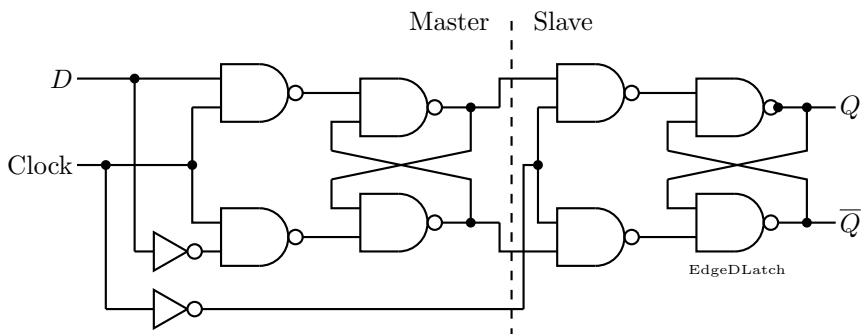


Figure 19: A neg Edge Triggered Master-Slave Flip Flop